
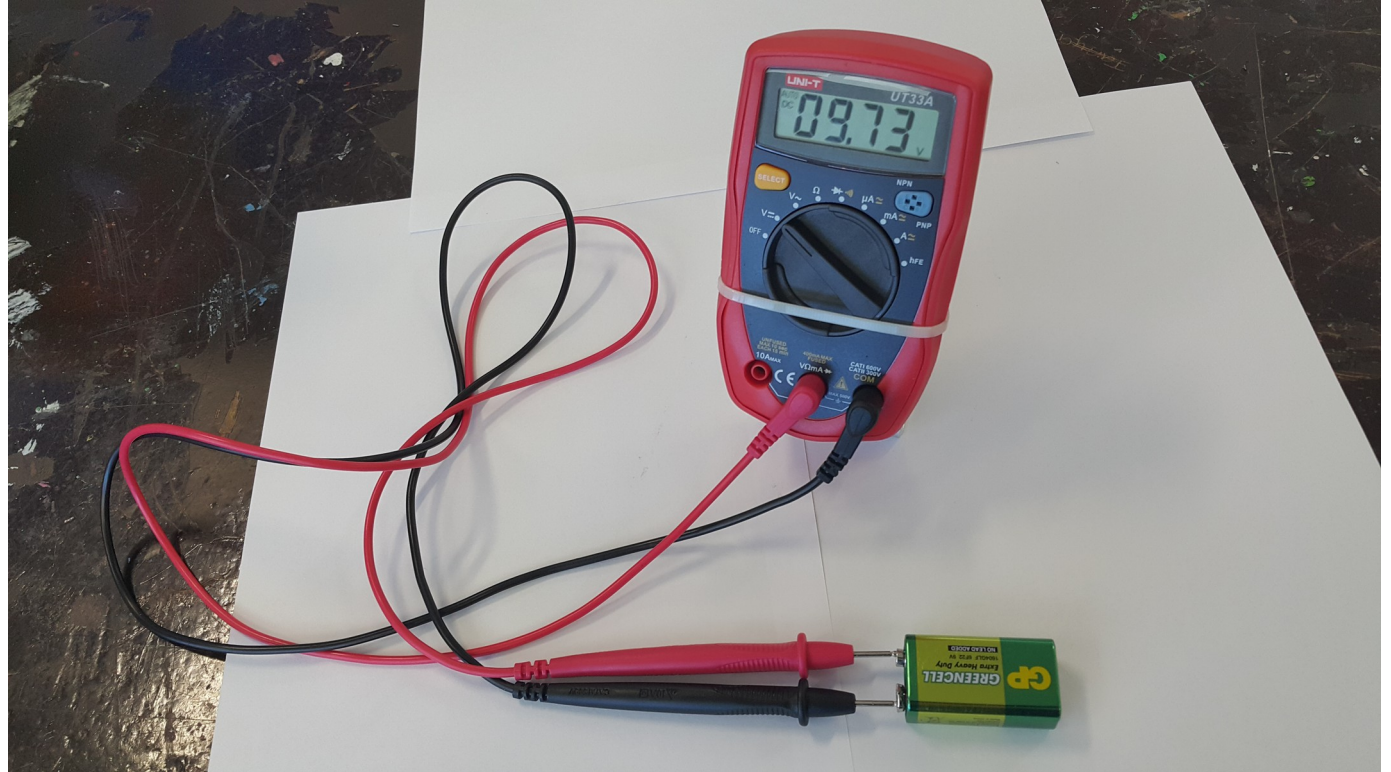


Using the multimeter


1- Measuring voltage across a battery

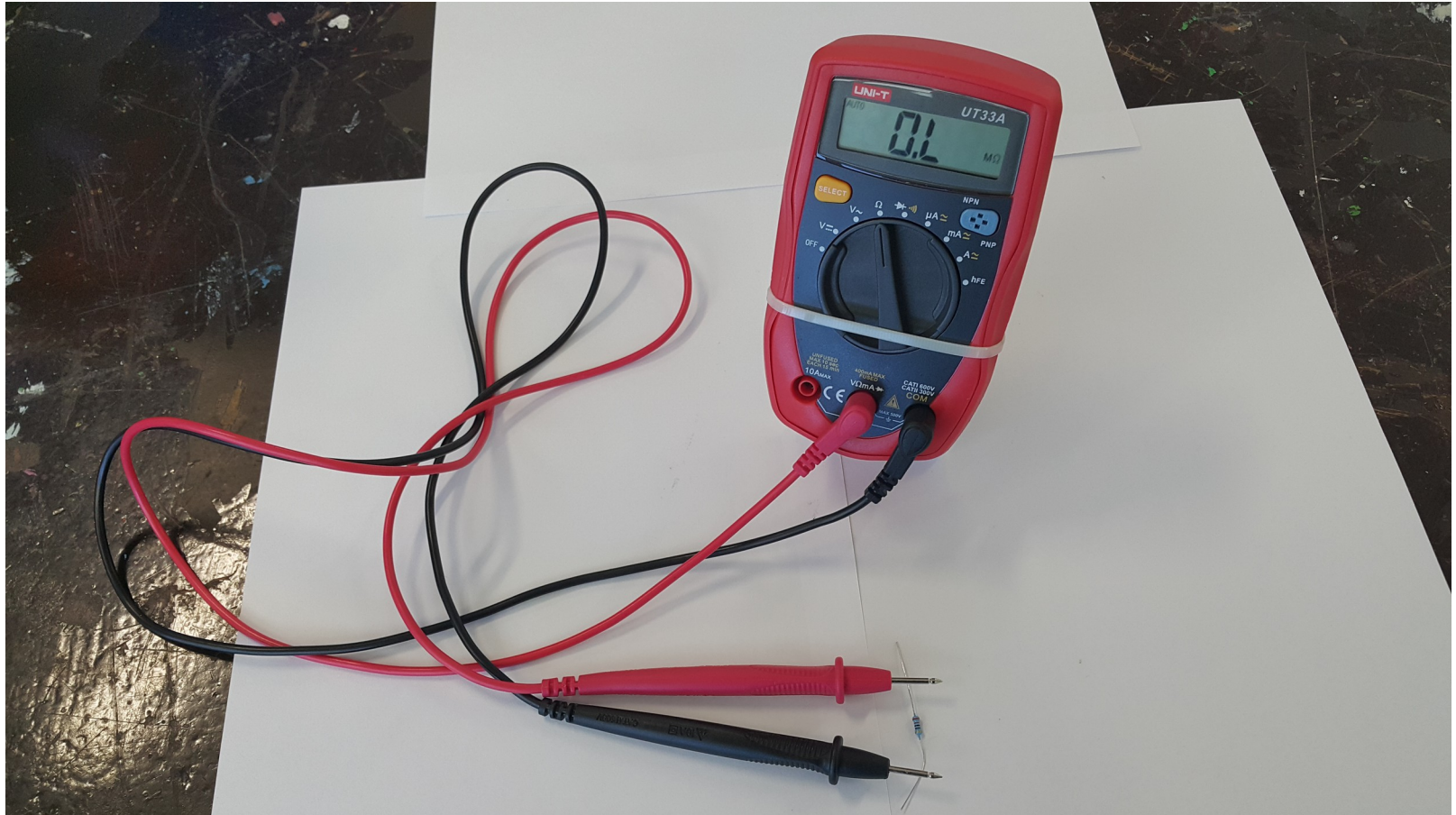


2- Measuring Resistance



3- Measuring Continuity Circuit

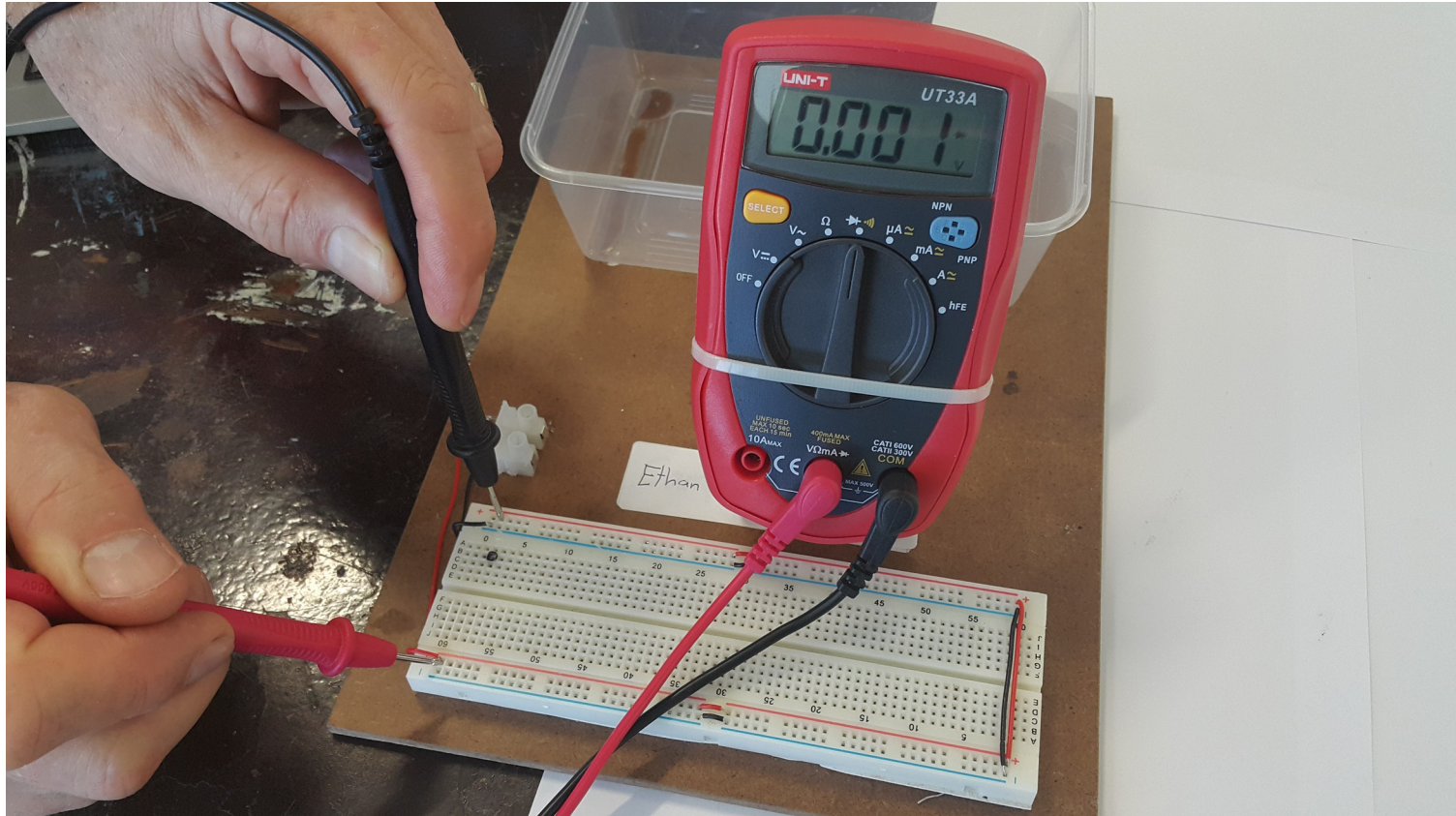

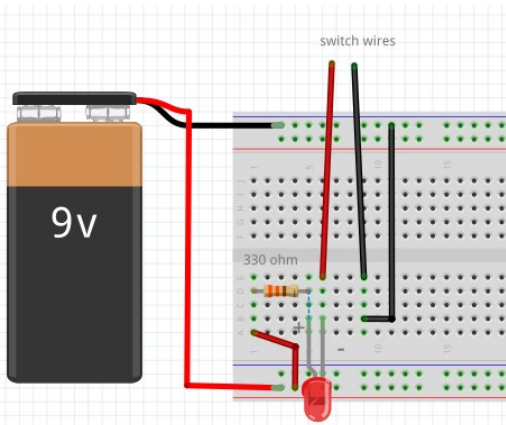
Basic Circuit and Transistor Circuit Measurements



Basic Circuit and Transistor Circuit Measurements

Follow the instructions on these slides to build your breadboard circuits, make the measurements and answer the questions

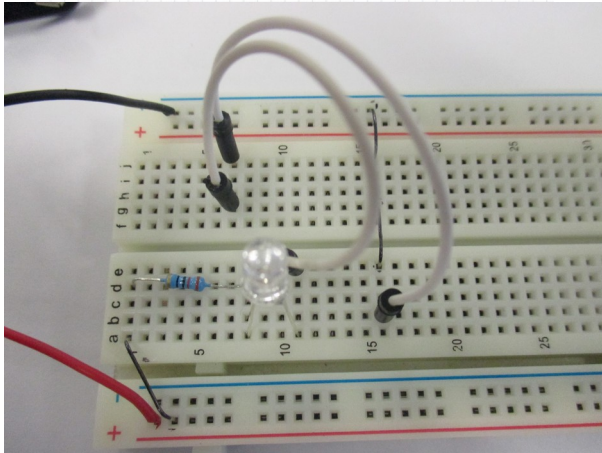- You can work together to make measurements using the multimeter, but you must **answer the questions individually**
- You can copy/paste the questions from these slides into your own slides (do not include the instructions given in these slides though)



Build the basic circuit on your breadboard using Tinkercad layout and the breadboard photo shown here as a guide (use a multimeter set to Ω to measure the resistor value)

- two hook-up wires are used for the switch, to enable the circuit to remain on the switch wires can be plugged into a common row as shown

photo of your
breadboard with
the basic circuit
here

Task 1:

Take a photo of your working breadboard and insert it into your slides

With your switch wires connected together and LED on, set your multimeter to measure voltage (**DC -**)

Measure the voltage across the LED

Voltage =

Measure the voltage across the 330 ohm resistor

Voltage =

Measure the voltage across the +ve and -ve rails (the battery voltage)

Voltage =

Add the voltage of the LED and resistor together

Voltage total =

Deduct the voltage total of the led/resistor from the battery voltage

The total voltage of the led/resistor should equal the battery voltage (within a few millivolts) does it?

If not, give a brief explanation of why this may be

