
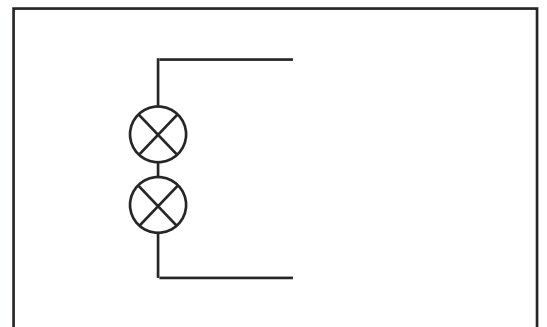
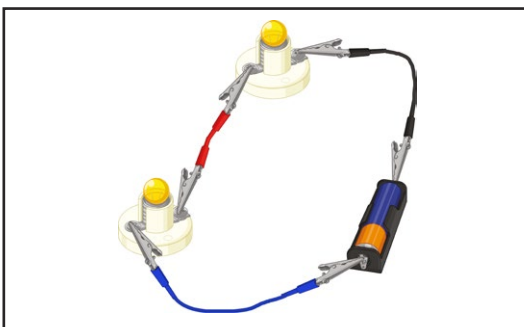
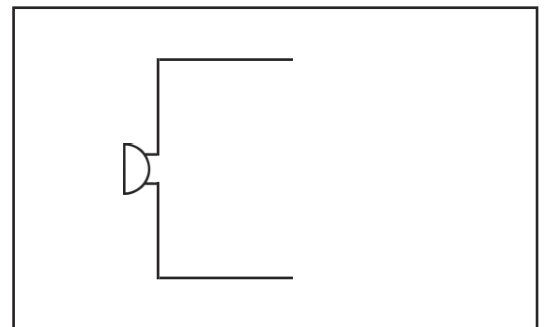
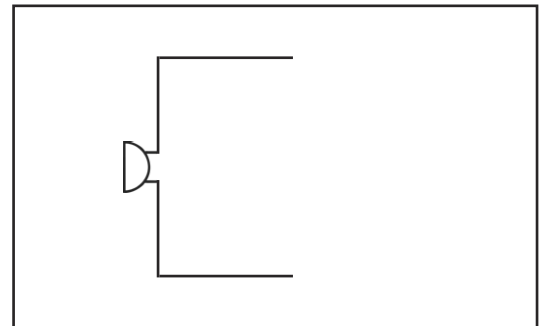
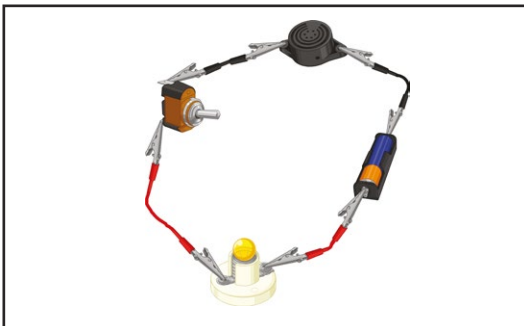
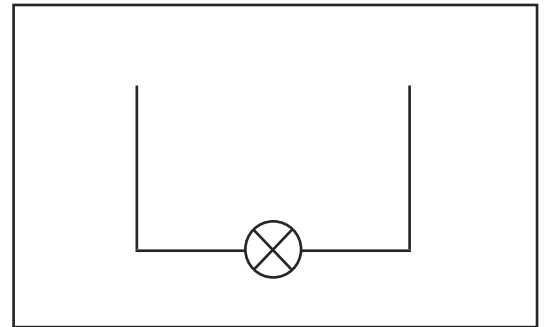
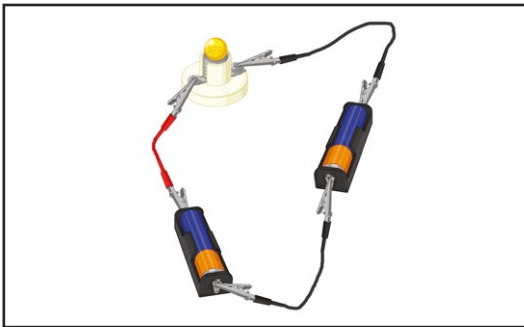
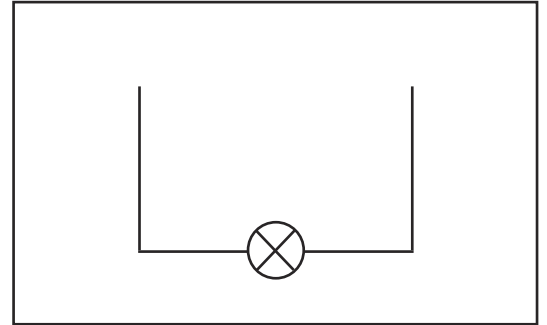


# Drawing Circuit Diagrams

For each of the five pictures below, complete the corresponding circuit diagram using symbols.

Remember to use a pencil and ruler.

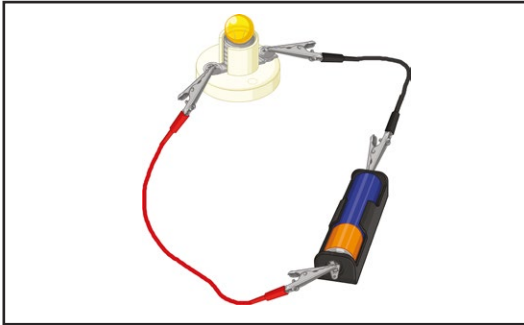

# Drawing Circuit Diagrams Answers

For each of the five pictures below, complete the corresponding circuit diagram using symbols.

Remember to use a pencil and ruler.

