
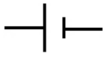


Drawing circuit diagrams

a) Draw a line to match each symbol with its correct name. One name is not needed.

Symbol

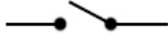

Name

- fuse
- bell
- cell
- lamp
- wire
- closed switch
- battery
- open switch

b) Use the symbols to draw a circuit which has a:

- battery
- bell and a lamp in series
- switch that is open

Circuit Drawing