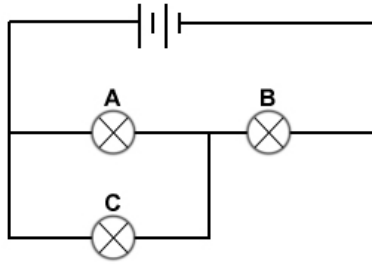


Parallel and series



Use the circuit above to answer the following questions.

a) Which bulbs are in parallel? _____

b) Which bulbs are in series? _____

c) If all the bulbs have the same resistance, which bulbs would have the same current flowing through them?

d) Draw a switch in the circuit above so that bulb A can be turned off when bulb C and bulb B are still going.

Published on *Assessment Resource Banks* (<https://arbs.nzcer.org.nz>)